

# Math 307 Lecture 17

## Forced Vibrations

W.R. Casper

Department of Mathematics  
University of Washington

May 14, 2014

# Today!

## Last time:

- More on Mechanical and Electrical Vibrations

## This time:

- Forced vibrations

## Next time:

- Review for final exam

# Today!

Last time:

- More on Mechanical and Electrical Vibrations

This time:

- Forced vibrations

Next time:

- Review for final exam

# Today!

Last time:

- More on Mechanical and Electrical Vibrations

This time:

- Forced vibrations

Next time:

- Review for final exam

# Today!

Last time:

- More on Mechanical and Electrical Vibrations

This time:

- Forced vibrations

Next time:

- Review for final exam

# Today!

Last time:

- More on Mechanical and Electrical Vibrations

This time:

- Forced vibrations

Next time:

- Review for final exam

# Today!

Last time:

- More on Mechanical and Electrical Vibrations

This time:

- Forced vibrations

Next time:

- Review for final exam

# Outline

- 1 **Forced Vibrations Introduction**
  - First Examples
  - Alternating Current and LCR Circuits
- 2 **Forced Vibration Example**
  - LCR Circuit Specific Example
  - DC Case
  - AC Case



# Outline

- 1 **Forced Vibrations Introduction**
  - **First Examples**
  - Alternating Current and LCR Circuits
  
- 2 **Forced Vibration Example**
  - LCR Circuit Specific Example
  - DC Case
  - AC Case

# What is Forced Vibration?

- Forced vibration is what occurs when we have an equation of the form

$$ay'' + by' + cy = R \cos(\omega t).$$

- where  $a, b, c$  are positive constants
- Intuitively, we should think about a spring with an external periodic force applied.
- What solutions look like depend very strongly on the values of  $a, b, c, R$ , and  $\omega$
- Today we will look at behavior when  $b > 0$
- Later we will study separately the case when  $b = 0$

# What is Forced Vibration?

- Forced vibration is what occurs when we have an equation of the form

$$ay'' + by' + cy = R \cos(\omega t).$$

- where  $a, b, c$  are positive constants
- Intuitively, we should think about a spring with an external periodic force applied.
- What solutions look like depend very strongly on the values of  $a, b, c, R$ , and  $\omega$
- Today we will look at behavior when  $b > 0$
- Later we will study separately the case when  $b = 0$

# What is Forced Vibration?

- Forced vibration is what occurs when we have an equation of the form

$$ay'' + by' + cy = R \cos(\omega t).$$

- where  $a, b, c$  are positive constants
- Intuitively, we should think about a spring with an external periodic force applied.
- What solutions look like depend very strongly on the values of  $a, b, c, R$ , and  $\omega$
- Today we will look at behavior when  $b > 0$
- Later we will study separately the case when  $b = 0$

# What is Forced Vibration?

- Forced vibration is what occurs when we have an equation of the form

$$ay'' + by' + cy = R \cos(\omega t).$$

- where  $a, b, c$  are positive constants
- Intuitively, we should think about a spring with an external periodic force applied.
- What solutions look like depend very strongly on the values of  $a, b, c, R$ , and  $\omega$
- Today we will look at behavior when  $b > 0$
- Later we will study separately the case when  $b = 0$



# Examples of Forced Vibration

- Forced vibrations occur naturally all the time!
- For example one could think of
  - A mass-spring system, with an external force applied
  - A LCR-circuit, where the voltage input  $E(t)$  is not constant
- What does forced vibration look like in comparison to unforced vibration?
- How does forced vibration behave at large timescales?

# Examples of Forced Vibration

- **Forced vibrations occur naturally all the time!**
- For example one could think of
  - A mass-spring system, with an external force applied
  - A LCR-circuit, where the voltage input  $E(t)$  is not constant
- What does forced vibration look like in comparison to unforced vibration?
- How does forced vibration behave at large timescales?

# Examples of Forced Vibration

- Forced vibrations occur naturally all the time!
- For example one could think of
  - A mass-spring system, with an external force applied
  - A LCR-circuit, where the voltage input  $E(t)$  is not constant
- What does forced vibration look like in comparison to unforced vibration?
- How does forced vibration behave at large timescales?

# Examples of Forced Vibration

- Forced vibrations occur naturally all the time!
- For example one could think of
  - A mass-spring system, with an external force applied
  - A LCR-circuit, where the voltage input  $E(t)$  is not constant
- What does forced vibration look like in comparison to unforced vibration?
- How does forced vibration behave at large timescales?

# Examples of Forced Vibration

- Forced vibrations occur naturally all the time!
- For example one could think of
  - A mass-spring system, with an external force applied
  - A LCR-circuit, where the voltage input  $E(t)$  is not constant
- What does forced vibration look like in comparison to unforced vibration?
- How does forced vibration behave at large timescales?

# Examples of Forced Vibration

- Forced vibrations occur naturally all the time!
- For example one could think of
  - A mass-spring system, with an external force applied
  - A LCR-circuit, where the voltage input  $E(t)$  is not constant
- What does forced vibration look like in comparison to unforced vibration?
- How does forced vibration behave at large timescales?

# Examples of Forced Vibration

- Forced vibrations occur naturally all the time!
- For example one could think of
  - A mass-spring system, with an external force applied
  - A LCR-circuit, where the voltage input  $E(t)$  is not constant
- What does forced vibration look like in comparison to unforced vibration?
- How does forced vibration behave at large timescales?

# Examples of Forced Vibration

- Forced vibrations occur naturally all the time!
- For example one could think of
  - A mass-spring system, with an external force applied
  - A LCR-circuit, where the voltage input  $E(t)$  is not constant
- What does forced vibration look like in comparison to unforced vibration?
- How does forced vibration behave at large timescales?



# Outline

- 1 **Forced Vibrations Introduction**
  - First Examples
  - **Alternating Current and LCR Circuits**
  
- 2 **Forced Vibration Example**
  - LCR Circuit Specific Example
  - DC Case
  - AC Case

## LCR-circuit example

- Last class, we found that the current in an LCR-circuit with inductance  $L$ , capacitance  $C$ , and resistance  $R$  (all positive constants) satisfies the second-order equation

$$LI'' + RI' + I/C = E'(t)$$

- where here  $E(t)$  is the voltage input into the LCR circuit by some power source
- power source could be a battery, or similar device
- could also be power from an electrical outlet or a motor with or without an alternator

## LCR-circuit example

- Last class, we found that the current in an LCR-circuit with inductance  $L$ , capacitance  $C$ , and resistance  $R$  (all positive constants) satisfies the second-order equation

$$LI'' + RI' + I/C = E'(t)$$

- where here  $E(t)$  is the voltage input into the LCR circuit by some power source
- power source could be a battery, or similar device
- could also be power from an electrical outlet or a motor with or without an alternator

# LCR-circuit example

- Last class, we found that the current in an LCR-circuit with inductance  $L$ , capacitance  $C$ , and resistance  $R$  (all positive constants) satisfies the second-order equation

$$LI'' + RI' + I/C = E'(t)$$

- where here  $E(t)$  is the voltage input into the LCR circuit by some power source
  - power source could be a battery, or similar device
  - could also be power from an electrical outlet or a motor with or without an alternator

## LCR-circuit example

- Last class, we found that the current in an LCR-circuit with inductance  $L$ , capacitance  $C$ , and resistance  $R$  (all positive constants) satisfies the second-order equation

$$LI'' + RI' + I/C = E'(t)$$

- where here  $E(t)$  is the voltage input into the LCR circuit by some power source
- power source could be a battery, or similar device
- could also be power from an electrical outlet or a motor with or without an alternator

## LCR-circuit example

- Last class, we found that the current in an LCR-circuit with inductance  $L$ , capacitance  $C$ , and resistance  $R$  (all positive constants) satisfies the second-order equation

$$LI'' + RI' + I/C = E'(t)$$

- where here  $E(t)$  is the voltage input into the LCR circuit by some power source
- power source could be a battery, or similar device
- could also be power from an electrical outlet or a motor with or without an alternator

## LCR-circuit example

- Suppose that our voltage source is  $V_0$  volts
- Depending on the kind of source, this may mean two different things
- If the source is a battery, then the voltage is *direct* and  $E(t) = V_0$ , so that  $E'(t) = 0$
- If the source is a wall outlet or alternator, the voltage is *alternating*
- In this case  $V_0$  typically refers to the *rms voltage*, so that the true voltage input is  $E(t) = \sqrt{2}V_0 \sin(\omega t)$ , where  $\omega$  is the electrical angular frequency of the power source
- For wall outlets in the U.S.A.,  $\omega/2\pi = 60$  Hz

## LCR-circuit example

- Suppose that our voltage source is  $V_0$  volts
- Depending on the kind of source, this may mean two different things
- If the source is a battery, then the voltage is *direct* and  $E(t) = V_0$ , so that  $E'(t) = 0$
- If the source is a wall outlet or alternator, the voltage is *alternating*
- In this case  $V_0$  typically refers to the *rms voltage*, so that the true voltage input is  $E(t) = \sqrt{2}V_0 \sin(\omega t)$ , where  $\omega$  is the electrical angular frequency of the power source
- For wall outlets in the U.S.A.,  $\omega/2\pi = 60$  Hz



# LCR-circuit example

- Suppose that our voltage source is  $V_0$  volts
- Depending on the kind of source, this may mean two different things
- If the source is a battery, then the voltage is *direct* and  $E(t) = V_0$ , so that  $E'(t) = 0$
- If the source is a wall outlet or alternator, the voltage is *alternating*
- In this case  $V_0$  typically refers to the *rms voltage*, so that the true voltage input is  $E(t) = \sqrt{2} V_0 \sin(\omega t)$ , where  $\omega$  is the electrical angular frequency of the power source
- For wall outlets in the U.S.A.,  $\omega/2\pi = 60$  Hz

# LCR-circuit example

- Suppose that our voltage source is  $V_0$  volts
- Depending on the kind of source, this may mean two different things
- If the source is a battery, then the voltage is *direct* and  $E(t) = V_0$ , so that  $E'(t) = 0$
- If the source is a wall outlet or alternator, the voltage is *alternating*
- In this case  $V_0$  typically refers to the *rms voltage*, so that the true voltage input is  $E(t) = \sqrt{2} V_0 \sin(\omega t)$ , where  $\omega$  is the electrical angular frequency of the power source
- For wall outlets in the U.S.A.,  $\omega/2\pi = 60$  Hz

# LCR-circuit example

- Suppose that our voltage source is  $V_0$  volts
- Depending on the kind of source, this may mean two different things
- If the source is a battery, then the voltage is *direct* and  $E(t) = V_0$ , so that  $E'(t) = 0$
- If the source is a wall outlet or alternator, the voltage is *alternating*
- In this case  $V_0$  typically refers to the *rms voltage*, so that the true voltage input is  $E(t) = \sqrt{2} V_0 \sin(\omega t)$ , where  $\omega$  is the electrical angular frequency of the power source
- For wall outlets in the U.S.A.,  $\omega/2\pi = 60$  Hz

# LCR-circuit example

- Suppose that our voltage source is  $V_0$  volts
- Depending on the kind of source, this may mean two different things
- If the source is a battery, then the voltage is *direct* and  $E(t) = V_0$ , so that  $E'(t) = 0$
- If the source is a wall outlet or alternator, the voltage is *alternating*
- In this case  $V_0$  typically refers to the *rms voltage*, so that the true voltage input is  $E(t) = \sqrt{2}V_0 \sin(\omega t)$ , where  $\omega$  is the electrical angular frequency of the power source
- For wall outlets in the U.S.A.,  $\omega/2\pi = 60$  Hz

# LCR-circuit example

- Suppose that our voltage source is  $V_0$  volts
- Depending on the kind of source, this may mean two different things
- If the source is a battery, then the voltage is *direct* and  $E(t) = V_0$ , so that  $E'(t) = 0$
- If the source is a wall outlet or alternator, the voltage is *alternating*
- In this case  $V_0$  typically refers to the *rms voltage*, so that the true voltage input is  $E(t) = \sqrt{2}V_0 \sin(\omega t)$ , where  $\omega$  is the electrical angular frequency of the power source
- For wall outlets in the U.S.A.,  $\omega/2\pi = 60$  Hz

# LCR-circuit: direct current case

- Suppose that our voltage source is  $V_0$  volts in direct current (ie. from a battery or DC generator)
- Then  $E(t)$  is constant, so  $E'(t) = 0$
- Also assume that  $R > 0$  (which is *always* true in real life)
- The current satisfies the equation

$$LI'' + RI' + I/C = 0$$

- and for  $R^2 < 4L/C$ , the solution is of the form

$$I = re^{-Rt/2L} \cos(\mu t - \delta)$$

- where  $\mu = (\sqrt{R^2 - 4L/C})/2L$ , and  $r, \delta$  are constants depending on the initial conditions  $I(0)$  and  $I'(0)$

# LCR-circuit: direct current case

- Suppose that our voltage source is  $V_0$  volts in direct current (ie. from a battery or DC generator)
- Then  $E(t)$  is constant, so  $E'(t) = 0$
- Also assume that  $R > 0$  (which is *always* true in real life)
- The current satisfies the equation

$$LI'' + RI' + I/C = 0$$

- and for  $R^2 < 4L/C$ , the solution is of the form

$$I = re^{-Rt/2L} \cos(\mu t - \delta)$$

- where  $\mu = (\sqrt{R^2 - 4L/C})/2L$ , and  $r, \delta$  are constants depending on the initial conditions  $I(0)$  and  $I'(0)$

# LCR-circuit: direct current case

- Suppose that our voltage source is  $V_0$  volts in direct current (ie. from a battery or DC generator)
- Then  $E(t)$  is constant, so  $E'(t) = 0$
- Also assume that  $R > 0$  (which is *always* true in real life)
- The current satisfies the equation

$$LI'' + RI' + I/C = 0$$

- and for  $R^2 < 4L/C$ , the solution is of the form

$$I = re^{-Rt/2L} \cos(\mu t - \delta)$$

- where  $\mu = (\sqrt{R^2 - 4L/C})/2L$ , and  $r, \delta$  are constants depending on the initial conditions  $I(0)$  and  $I'(0)$

# LCR-circuit: direct current case

- Suppose that our voltage source is  $V_0$  volts in direct current (ie. from a battery or DC generator)
- Then  $E(t)$  is constant, so  $E'(t) = 0$
- Also assume that  $R > 0$  (which is *always* true in real life)
- The current satisfies the equation

$$LI'' + RI' + I/C = 0$$

- and for  $R^2 < 4L/C$ , the solution is of the form

$$I = re^{-Rt/2L} \cos(\mu t - \delta)$$

- where  $\mu = (\sqrt{R^2 - 4L/C})/2L$ , and  $r, \delta$  are constants depending on the initial conditions  $I(0)$  and  $I'(0)$

# LCR-circuit: direct current case

- How does  $I(t)$  behave at large time?
- It becomes very small, approaching zero exponentially fast
- Comparatively, the behavior of the current in the alternating voltage source case is much more interesting

# LCR-circuit: direct current case

- How does  $I(t)$  behave at large time?
- It becomes very small, approaching zero exponentially fast
- Comparatively, the behavior of the current in the alternating voltage source case is much more interesting

## LCR-circuit: direct current case

- How does  $I(t)$  behave at large time?
- It becomes very small, approaching zero exponentially fast
- Comparatively, the behavior of the current in the alternating voltage source case is much more interesting

## LCR-circuit: direct current case

- How does  $I(t)$  behave at large time?
- It becomes very small, approaching zero exponentially fast
- Comparatively, the behavior of the current in the alternating voltage source case is much more interesting



# LCR-circuit: alternating current case

- Suppose that our voltage source is  $V_0$  volts in alternating current (ie. from a wall socket or alternator)
- Then  $E(t) = \sqrt{2} V_0 \sin(\omega t)$ , so  $E'(t) = \sqrt{2} \omega V_0 \cos(\omega t)$
- Also assume that  $R > 0$  (which is *always* true in real life)
- The current satisfies the equation

$$LI'' + RI' + I/C = \sqrt{2} \omega V_0 \cos(\omega t)$$

- In this case, the solution has two components

$$I = \underbrace{c_1 l_1 + c_2 l_2}_{\text{solution to homogeneous equation}} + \underbrace{l_p}_{\text{particular solution}}$$

- Where  $c_1, c_2$  are constants, depending on initial condition

# LCR-circuit: alternating current case

- Suppose that our voltage source is  $V_0$  volts in alternating current (ie. from a wall socket or alternator)
- Then  $E(t) = \sqrt{2}V_0 \sin(\omega t)$ , so  $E'(t) = \sqrt{2}\omega V_0 \cos(\omega t)$
- Also assume that  $R > 0$  (which is *always* true in real life)
- The current satisfies the equation

$$LI'' + RI' + I/C = \sqrt{2}\omega V_0 \cos(\omega t)$$

- In this case, the solution has two components

$$I = \underbrace{c_1 l_1 + c_2 l_2}_{\text{solution to homogeneous equation}} + \underbrace{l_p}_{\text{particular solution}}$$

- Where  $c_1, c_2$  are constants, depending on initial condition

# LCR-circuit: alternating current case

- Suppose that our voltage source is  $V_0$  volts in alternating current (ie. from a wall socket or alternator)
- Then  $E(t) = \sqrt{2}V_0 \sin(\omega t)$ , so  $E'(t) = \sqrt{2}\omega V_0 \cos(\omega t)$
- Also assume that  $R > 0$  (which is *always* true in real life)
- The current satisfies the equation

$$LI'' + RI' + I/C = \sqrt{2}\omega V_0 \cos(\omega t)$$

- In this case, the solution has two components

$$I = \underbrace{c_1 l_1 + c_2 l_2}_{\text{solution to homogeneous equation}} + \underbrace{l_p}_{\text{particular solution}}$$

- Where  $c_1, c_2$  are constants, depending on initial condition

# LCR-circuit: alternating current case

- Suppose that our voltage source is  $V_0$  volts in alternating current (ie. from a wall socket or alternator)
- Then  $E(t) = \sqrt{2}V_0 \sin(\omega t)$ , so  $E'(t) = \sqrt{2}\omega V_0 \cos(\omega t)$
- Also assume that  $R > 0$  (which is *always* true in real life)
- The current satisfies the equation

$$LI'' + RI' + I/C = \sqrt{2}\omega V_0 \cos(\omega t)$$

- In this case, the solution has two components

$$I = \underbrace{c_1 l_1 + c_2 l_2}_{\text{solution to homogeneous equation}} + \underbrace{l_p}_{\text{particular solution}}$$

- Where  $c_1, c_2$  are constants, depending on initial condition

# LCR-circuit: alternating current case

- Suppose that our voltage source is  $V_0$  volts in alternating current (ie. from a wall socket or alternator)
- Then  $E(t) = \sqrt{2}V_0 \sin(\omega t)$ , so  $E'(t) = \sqrt{2}\omega V_0 \cos(\omega t)$
- Also assume that  $R > 0$  (which is *always* true in real life)
- The current satisfies the equation

$$LI'' + RI' + I/C = \sqrt{2}\omega V_0 \cos(\omega t)$$

- In this case, the solution has two components

$$I = \underbrace{c_1 l_1 + c_2 l_2}_{\text{solution to homogeneous equation}} + \underbrace{l_p}_{\text{particular solution}}$$

- Where  $c_1, c_2$  are constants, depending on initial condition

# LCR-circuit: alternating current case

- Suppose that our voltage source is  $V_0$  volts in alternating current (ie. from a wall socket or alternator)
- Then  $E(t) = \sqrt{2}V_0 \sin(\omega t)$ , so  $E'(t) = \sqrt{2}\omega V_0 \cos(\omega t)$
- Also assume that  $R > 0$  (which is *always* true in real life)
- The current satisfies the equation

$$LI'' + RI' + I/C = \sqrt{2}\omega V_0 \cos(\omega t)$$

- In this case, the solution has two components

$$I = \underbrace{c_1 I_1 + c_2 I_2}_{\text{solution to homogeneous equation}} + \underbrace{I_p}_{\text{particular solution}}$$

- Where  $c_1, c_2$  are constants, depending on initial condition

# LCR-circuit: alternating current case

- Suppose that our voltage source is  $V_0$  volts in alternating current (ie. from a wall socket or alternator)
- Then  $E(t) = \sqrt{2}V_0 \sin(\omega t)$ , so  $E'(t) = \sqrt{2}\omega V_0 \cos(\omega t)$
- Also assume that  $R > 0$  (which is *always* true in real life)
- The current satisfies the equation

$$LI'' + RI' + I/C = \sqrt{2}\omega V_0 \cos(\omega t)$$

- In this case, the solution has two components

$$I = \underbrace{c_1 I_1 + c_2 I_2}_{\text{solution to homogeneous equation}} + \underbrace{I_p}_{\text{particular solution}}$$

- Where  $c_1, c_2$  are constants, depending on initial condition

## LCR-circuit: alternating current case

- As the solution to the homogeneous equation we derived before shows us, the solution to the homogeneous equation will become very small at large times
- Therefore, at large times, the general solution will look very similar to the particular solution
- For this reason, we often call  $c_1 I_1 + c_2 I_2$  the *transient solution* (in the case of circuits, also called a transient current)
- And we call  $I_p$  the *steady state solution* or *forced response* (in the circuit case, also called *steady state current*).



## LCR-circuit: alternating current case

- As the solution to the homogeneous equation we derived before shows us, the solution to the homogeneous equation will become very small at large times
- Therefore, at large times, the general solution will look very similar to the particular solution
- For this reason, we often call  $c_1 I_1 + c_2 I_2$  the *transient solution* (in the case of circuits, also called a transient current)
- And we call  $I_p$  the *steady state solution* or *forced response* (in the circuit case, also called *steady state current*).

## LCR-circuit: alternating current case

- As the solution to the homogeneous equation we derived before shows us, the solution to the homogeneous equation will become very small at large times
- Therefore, at large times, the general solution will look very similar to the particular solution
- For this reason, we often call  $c_1 I_1 + c_2 I_2$  the *transient solution* (in the case of circuits, also called a transient current)
- And we call  $I_p$  the *steady state solution* or *forced response* (in the circuit case, also called *steady state current*).

## LCR-circuit: alternating current case

- As the solution to the homogeneous equation we derived before shows us, the solution to the homogeneous equation will become very small at large times
- Therefore, at large times, the general solution will look very similar to the particular solution
- For this reason, we often call  $c_1 I_1 + c_2 I_2$  the *transient solution* (in the case of circuits, also called a transient current)
- And we call  $I_p$  the *steady state solution* or *forced response* (in the circuit case, also called *steady state current*).

## LCR-circuit: alternating current case

- As the solution to the homogeneous equation we derived before shows us, the solution to the homogeneous equation will become very small at large times
- Therefore, at large times, the general solution will look very similar to the particular solution
- For this reason, we often call  $c_1 I_1 + c_2 I_2$  the *transient solution* (in the case of circuits, also called a transient current)
- And we call  $I_p$  the *steady state solution* or *forced response* (in the circuit case, also called *steady state current*).

# LCR-circuit: alternating current case

- Thus we write

$$I = I_{\text{transient}} + I_{\text{steady}},$$

- where  $I_{\text{steady}}$  is a particular solution of

$$LI'' + RI' + I/C = \sqrt{2}\omega V_0 \cos(\omega t)$$

- and where  $I_{\text{transient}}$  is a solution of the corresponding homogeneous equation

$$LI'' + RI' + I/C = 0$$

- which we know get exponentially smaller as time increases when the resistance  $R$  is not zero

# LCR-circuit: alternating current case

- Thus we write

$$I = I_{\text{transient}} + I_{\text{steady}},$$

- where  $I_{\text{steady}}$  is a particular solution of

$$LI'' + RI' + I/C = \sqrt{2}\omega V_0 \cos(\omega t)$$

- and where  $I_{\text{transient}}$  is a solution of the corresponding homogeneous equation

$$LI'' + RI' + I/C = 0$$

- which we know get exponentially smaller as time increases when the resistance  $R$  is not zero

# LCR-circuit: alternating current case

- Thus we write

$$I = I_{\text{transient}} + I_{\text{steady}},$$

- where  $I_{\text{steady}}$  is a particular solution of

$$LI'' + RI' + I/C = \sqrt{2}\omega V_0 \cos(\omega t)$$

- and where  $I_{\text{transient}}$  is a solution of the corresponding homogeneous equation

$$LI'' + RI' + I/C = 0$$

- which we know get exponentially smaller as time increases when the resistance  $R$  is not zero

# LCR-circuit: alternating current case

- Thus we write

$$I = I_{\text{transient}} + I_{\text{steady}},$$

- where  $I_{\text{steady}}$  is a particular solution of

$$LI'' + RI' + I/C = \sqrt{2}\omega V_0 \cos(\omega t)$$

- and where  $I_{\text{transient}}$  is a solution of the corresponding homogeneous equation

$$LI'' + RI' + I/C = 0$$

- which we know get exponentially smaller as time increases when the resistance  $R$  is not zero



# LCR-circuit: alternating current case

- Thus we write

$$I = I_{\text{transient}} + I_{\text{steady}},$$

- where  $I_{\text{steady}}$  is a particular solution of

$$LI'' + RI' + I/C = \sqrt{2}\omega V_0 \cos(\omega t)$$

- and where  $I_{\text{transient}}$  is a solution of the corresponding homogeneous equation

$$LI'' + RI' + I/C = 0$$

- which we know get exponentially smaller as time increases when the resistance  $R$  is not zero

# LCR-circuit: alternating current case

- Straightforward but tedious algebraic calculation may be used to show

$$I_{\text{steady}} = r \cos(\omega t - \delta),$$

- where

$$r = \frac{\sqrt{2}\omega V_0}{\Delta}, \quad \cos(\delta) = \frac{L(\omega_0^2 - \omega^2)}{\Delta}, \quad \sin(\delta) = \frac{R\omega}{\Delta}$$

- and also

$$\Delta = \sqrt{L^2(\omega_0^2 - \omega^2)^2 + R^2\omega^2}, \quad \omega_0 = 1/\sqrt{LC}$$

- so as time goes on, the current behaves like a wave with frequency the same as the frequency of  $E'(t)$

# LCR-circuit: alternating current case

- Straightforward but tedious algebraic calculation may be used to show

$$I_{\text{steady}} = r \cos(\omega t - \delta),$$

- where

$$r = \frac{\sqrt{2}\omega V_0}{\Delta}, \quad \cos(\delta) = \frac{L(\omega_0^2 - \omega^2)}{\Delta}, \quad \sin(\delta) = \frac{R\omega}{\Delta}$$

- and also

$$\Delta = \sqrt{L^2(\omega_0^2 - \omega^2)^2 + R^2\omega^2}, \quad \omega_0 = 1/\sqrt{LC}$$

- so as time goes on, the current behaves like a wave with frequency the same as the frequency of  $E'(t)$

# LCR-circuit: alternating current case

- Straightforward but tedious algebraic calculation may be used to show

$$I_{\text{steady}} = r \cos(\omega t - \delta),$$

- where

$$r = \frac{\sqrt{2}\omega V_0}{\Delta}, \quad \cos(\delta) = \frac{L(\omega_0^2 - \omega^2)}{\Delta}, \quad \sin(\delta) = \frac{R\omega}{\Delta}$$

- and also

$$\Delta = \sqrt{L^2(\omega_0^2 - \omega^2)^2 + R^2\omega^2}, \quad \omega_0 = 1/\sqrt{LC}$$

- so as time goes on, the current behaves like a wave with frequency the same as the frequency of  $E'(t)$

# LCR-circuit: alternating current case

- Straightforward but tedious algebraic calculation may be used to show

$$I_{\text{steady}} = r \cos(\omega t - \delta),$$

- where

$$r = \frac{\sqrt{2}\omega V_0}{\Delta}, \quad \cos(\delta) = \frac{L(\omega_0^2 - \omega^2)}{\Delta}, \quad \sin(\delta) = \frac{R\omega}{\Delta}$$

- and also

$$\Delta = \sqrt{L^2(\omega_0^2 - \omega^2)^2 + R^2\omega^2}, \quad \omega_0 = 1/\sqrt{LC}$$

- so as time goes on, the current behaves like a wave with frequency the same as the frequency of  $E'(t)$

# LCR-circuit: alternating current case

- Straightforward but tedious algebraic calculation may be used to show

$$I_{\text{steady}} = r \cos(\omega t - \delta),$$

- where

$$r = \frac{\sqrt{2}\omega V_0}{\Delta}, \quad \cos(\delta) = \frac{L(\omega_0^2 - \omega^2)}{\Delta}, \quad \sin(\delta) = \frac{R\omega}{\Delta}$$

- and also

$$\Delta = \sqrt{L^2(\omega_0^2 - \omega^2)^2 + R^2\omega^2}, \quad \omega_0 = 1/\sqrt{LC}$$

- so as time goes on, the current behaves like a wave with frequency the same as the frequency of  $E'(t)$

# Outline

- 1 Forced Vibrations Introduction
  - First Examples
  - Alternating Current and LCR Circuits
- 2 **Forced Vibration Example**
  - **LCR Circuit Specific Example**
  - DC Case
  - AC Case

## LCR-circuit example

### Example

Suppose that an LCR-circuit has a 1 H inductor, a 1 F capacitor, and a  $0.125\Omega$  resistor. Also suppose that the initially  $I'(0) = 0$  and  $I(0) = 2$ . If a voltage source of 0.25 volts is connected, determine the current as a function of time.

We consider two cases:

- when the voltage source is direct current (DC)
- when the voltage source is alternating current (AC)



# LCR-circuit example

## Example

Suppose that an LCR-circuit has a 1 H inductor, a 1 F capacitor, and a  $0.125\Omega$  resistor. Also suppose that the initially  $I'(0) = 0$  and  $I(0) = 2$ . If a voltage source of 0.25 volts is connected, determine the current as a function of time.

We consider two cases:

- when the voltage source is direct current (DC)
- when the voltage source is alternating current (AC)

# LCR-circuit example

## Example

Suppose that an LCR-circuit has a 1 H inductor, a 1 F capacitor, and a  $0.125\Omega$  resistor. Also suppose that the initially  $I'(0) = 0$  and  $I(0) = 2$ . If a voltage source of 0.25 volts is connected, determine the current as a function of time.

We consider two cases:

- when the voltage source is direct current (DC)
- when the voltage source is alternating current (AC)

## LCR-circuit example

### Example

Suppose that an LCR-circuit has a 1 H inductor, a 1 F capacitor, and a  $0.125\Omega$  resistor. Also suppose that the initially  $I'(0) = 0$  and  $I(0) = 2$ . If a voltage source of 0.25 volts is connected, determine the current as a function of time.

We consider two cases:

- when the voltage source is direct current (DC)
- when the voltage source is alternating current (AC)

# Outline

- 1 Forced Vibrations Introduction
  - First Examples
  - Alternating Current and LCR Circuits
- 2 Forced Vibration Example
  - LCR Circuit Specific Example
  - DC Case
  - AC Case

# LCR-circuit example: DC case

- Assume that the voltage source is direct
- We have that  $C = 1$ ,  $L = 1$ , and  $R = 0.125$ .
- In this case,  $E(t) = 0.25$ ,  $E'(0) = 0$ , so that  $I$  is a solution to the initial value problem

$$I'' + 0.125I' + I = 0, \quad I(0) = 2, \quad I'(0) = 0$$

- We solved this last time, and got

$$I = \frac{32}{\sqrt{255}} e^{-t/16} \cos\left(\frac{\sqrt{255}}{16}t - \delta\right)$$

$$\text{for } \delta = \tan^{-1} \frac{1}{\sqrt{255}} \approx 0.0625$$

# LCR-circuit example: DC case

- Assume that the voltage source is direct
- We have that  $C = 1$ ,  $L = 1$ , and  $R = 0.125$ .
- In this case,  $E(t) = 0.25$ ,  $E'(0) = 0$ , so that  $I$  is a solution to the initial value problem

$$I'' + 0.125I' + I = 0, \quad I(0) = 2, \quad I'(0) = 0$$

- We solved this last time, and got

$$I = \frac{32}{\sqrt{255}} e^{-t/16} \cos\left(\frac{\sqrt{255}}{16} t - \delta\right)$$

$$\text{for } \delta = \tan^{-1} \frac{1}{\sqrt{255}} \approx 0.0625$$

# LCR-circuit example: DC case

- Assume that the voltage source is direct
- We have that  $C = 1$ ,  $L = 1$ , and  $R = 0.125$ .
- In this case,  $E(t) = 0.25$ ,  $E'(0) = 0$ , so that  $I$  is a solution to the initial value problem

$$I'' + 0.125I' + I = 0, \quad I(0) = 2, \quad I'(0) = 0$$

- We solved this last time, and got

$$I = \frac{32}{\sqrt{255}} e^{-t/16} \cos\left(\frac{\sqrt{255}}{16} t - \delta\right)$$

$$\text{for } \delta = \tan^{-1} \frac{1}{\sqrt{255}} \approx 0.0625$$

# LCR-circuit example: DC case

- Assume that the voltage source is direct
- We have that  $C = 1$ ,  $L = 1$ , and  $R = 0.125$ .
- In this case,  $E(t) = 0.25$ ,  $E'(0) = 0$ , so that  $I$  is a solution to the initial value problem

$$I'' + 0.125I' + I = 0, \quad I(0) = 2, \quad I'(0) = 0$$

- We solved this last time, and got

$$I = \frac{32}{\sqrt{255}} e^{-t/16} \cos\left(\frac{\sqrt{255}}{16} t - \delta\right)$$

$$\text{for } \delta = \tan^{-1} \frac{1}{\sqrt{255}} \approx 0.0625$$



# LCR-circuit example: DC case

- Assume that the voltage source is direct
- We have that  $C = 1$ ,  $L = 1$ , and  $R = 0.125$ .
- In this case,  $E(t) = 0.25$ ,  $E'(0) = 0$ , so that  $I$  is a solution to the initial value problem

$$I'' + 0.125I' + I = 0, \quad I(0) = 2, \quad I'(0) = 0$$


- We solved this last time, and got

$$I = \frac{32}{\sqrt{255}} e^{-t/16} \cos\left(\frac{\sqrt{255}}{16}t - \delta\right)$$

$$\text{for } \delta = \tan^{-1} \frac{1}{\sqrt{255}} \approx 0.0625$$

# LCR-circuit example: DC case

Figure : Current in the LCR circuit  $L = 1$ ,  $C = 1$ ,  $R = 0.125$ ,  $E = 0.25$ , with the initial condition  $I(0) = 2$  and  $I'(0) = 0$

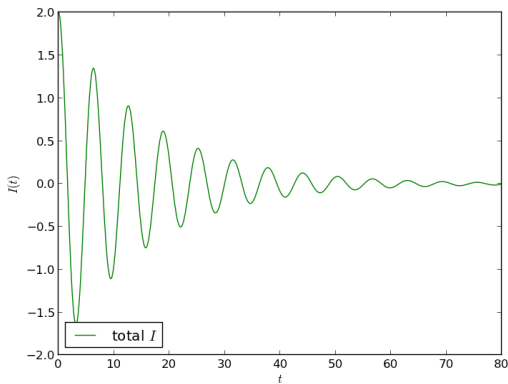

# Outline

- 1 Forced Vibrations Introduction
  - First Examples
  - Alternating Current and LCR Circuits
- 2 **Forced Vibration Example**
  - LCR Circuit Specific Example
  - DC Case
  - **AC Case**

# LCR-circuit example: AC case

- Assume the voltage source is alternating with angular frequency  $\omega = 1$
- We have that  $C = 1$ ,  $L = 1$ , and  $R = 0.125$ .
- In this case, it's the RMS voltage that is 0.25 volts
- This means that  $E(t) = 0.25\sqrt{2} \sin(t)$ , and  $E'(0) = 0.25\sqrt{2} \cos(t)$ , so that  $I$  is a solution to the initial value problem

$$I'' + 0.125I' + I = 0.25\sqrt{2} \cos(t)$$

# LCR-circuit example: AC case

- Assume the voltage source is alternating with angular frequency  $\omega = 1$
- We have that  $C = 1$ ,  $L = 1$ , and  $R = 0.125$ .
- In this case, it's the RMS voltage that is 0.25 volts
- This means that  $E(t) = 0.25\sqrt{2} \sin(t)$ , and  $E'(0) = 0.25\sqrt{2} \cos(t)$ , so that  $I$  is a solution to the initial value problem

$$I'' + 0.125I' + I = 0.25\sqrt{2} \cos(t)$$

# LCR-circuit example: AC case

- Assume the voltage source is alternating with angular frequency  $\omega = 1$
- We have that  $C = 1$ ,  $L = 1$ , and  $R = 0.125$ .
- In this case, it's the RMS voltage that is 0.25 volts
- This means that  $E(t) = 0.25\sqrt{2} \sin(t)$ , and  $E'(0) = 0.25\sqrt{2} \cos(t)$ , so that  $I$  is a solution to the initial value problem

$$I'' + 0.125I' + I = 0.25\sqrt{2} \cos(t)$$

# LCR-circuit example: AC case

- Assume the voltage source is alternating with angular frequency  $\omega = 1$
- We have that  $C = 1$ ,  $L = 1$ , and  $R = 0.125$ .
- In this case, it's the RMS voltage that is 0.25 volts
- This means that  $E(t) = 0.25\sqrt{2} \sin(t)$ , and  $E'(0) = 0.25\sqrt{2} \cos(t)$ , so that  $I$  is a solution to the initial value problem

$$I'' + 0.125I' + I = 0.25\sqrt{2} \cos(t)$$

# LCR-circuit example: AC case

- Assume the voltage source is alternating with angular frequency  $\omega = 1$
- We have that  $C = 1$ ,  $L = 1$ , and  $R = 0.125$ .
- In this case, it's the RMS voltage that is 0.25 volts
- This means that  $E(t) = 0.25\sqrt{2} \sin(t)$ , and  $E'(0) = 0.25\sqrt{2} \cos(t)$ , so that  $I$  is a solution to the initial value problem

$$I'' + 0.125I' + I = 0.25\sqrt{2} \cos(t)$$



# LCR-circuit example: AC case

- As per our previous discussion, we write

$$I = I_{\text{transient}} + I_{\text{stable}},$$

- where  $I_{\text{transient}}$  is a solution of the homogeneous equation

$$I'' + 0.125I' + I = 0$$

- and where  $I_{\text{stable}}$  is a particular solution of

$$I'' + 0.125I' + I = 0.25\sqrt{2} \cos(t)$$

# LCR-circuit example: AC case

- As per our previous discussion, we write

$$I = I_{\text{transient}} + I_{\text{stable}},$$

- where  $I_{\text{transient}}$  is a solution of the homogeneous equation

$$I'' + 0.125I' + I = 0$$

- and where  $I_{\text{stable}}$  is a particular solution of

$$I'' + 0.125I' + I = 0.25\sqrt{2}\cos(t)$$

# LCR-circuit example: AC case

- As per our previous discussion, we write

$$I = I_{\text{transient}} + I_{\text{stable}},$$

- where  $I_{\text{transient}}$  is a solution of the homogeneous equation

$$I'' + 0.125I' + I = 0$$

- and where  $I_{\text{stable}}$  is a particular solution of

$$I'' + 0.125I' + I = 0.25\sqrt{2}\cos(t)$$

# LCR-circuit example: AC case

- As per our previous discussion, we write

$$I = I_{\text{transient}} + I_{\text{stable}},$$

- where  $I_{\text{transient}}$  is a solution of the homogeneous equation

$$I'' + 0.125I' + I = 0$$

- and where  $I_{\text{stable}}$  is a particular solution of

$$I'' + 0.125I' + I = 0.25\sqrt{2}\cos(t)$$

# LCR-circuit example: AC case

- Using the equation of the previous slide,

$$I_{\text{steady}} = r \cos(\omega t - \delta),$$

- where  $\omega_0 = 1$ ,  $\Delta = \sqrt{0.125} = \sqrt{2}/4$ ,  $\delta = \pi/2$ , and  $r = 1$ , so that

$$I_{\text{steady}} = \cos\left(t - \frac{\pi}{2}\right)$$

# LCR-circuit example: AC case

- Using the equation of the previous slide,

$$I_{\text{steady}} = r \cos(\omega t - \delta),$$

- where  $\omega_0 = 1$ ,  $\Delta = \sqrt{0.125} = \sqrt{2}/4$ ,  $\delta = \pi/2$ , and  $r = 1$ , so that

$$I_{\text{steady}} = \cos\left(t - \frac{\pi}{2}\right)$$

# LCR-circuit example: AC case

- Using the equation of the previous slide,

$$I_{\text{steady}} = r \cos(\omega t - \delta),$$

- where  $\omega_0 = 1$ ,  $\Delta = \sqrt{0.125} = \sqrt{2}/4$ ,  $\delta = \pi/2$ , and  $r = 1$ , so that

$$I_{\text{steady}} = \cos\left(t - \frac{\pi}{2}\right)$$

# LCR-circuit example: AC case

- Also, since  $I_{\text{transient}}$  is a solution of the homogeneous equation, we know that

$$I_{\text{transient}} = r_0 e^{-t/16} \cos\left(\frac{\sqrt{255}}{16}t - \delta_0\right),$$

- where  $r_0$  and  $\delta_0$  are some constants depending on our initial condition  $I(0) = 2$  and  $I'(0) = 0$ .
- EXERCISE: determine  $r_0$  and  $\delta_0$



# LCR-circuit example: AC case

- Also, since  $I_{\text{transient}}$  is a solution of the homogeneous equation, we know that

$$I_{\text{transient}} = r_0 e^{-t/16} \cos\left(\frac{\sqrt{255}}{16}t - \delta_0\right),$$

- where  $r_0$  and  $\delta_0$  are some constants depending on our initial condition  $I(0) = 2$  and  $I'(0) = 0$ .
- EXERCISE: determine  $r_0$  and  $\delta_0$

# LCR-circuit example: AC case

- Also, since  $I_{\text{transient}}$  is a solution of the homogeneous equation, we know that

$$I_{\text{transient}} = r_0 e^{-t/16} \cos\left(\frac{\sqrt{255}}{16}t - \delta_0\right),$$

- where  $r_0$  and  $\delta_0$  are some constants depending on our initial condition  $I(0) = 2$  and  $I'(0) = 0$ .
- EXERCISE: determine  $r_0$  and  $\delta_0$

# LCR-circuit example: AC case


- Also, since  $I_{\text{transient}}$  is a solution of the homogeneous equation, we know that

$$I_{\text{transient}} = r_0 e^{-t/16} \cos\left(\frac{\sqrt{255}}{16}t - \delta_0\right),$$

- where  $r_0$  and  $\delta_0$  are some constants depending on our initial condition  $I(0) = 2$  and  $I'(0) = 0$ .
- EXERCISE: determine  $r_0$  and  $\delta_0$

# LCR-circuit example: AC case

Figure : Current in the LCR circuit  $L = 1$ ,  $C = 1$ ,  $R = 0.125$ ,  $E = 0.25$ , with the initial condition  $I(0) = 2$  and  $I'(0) = 0$

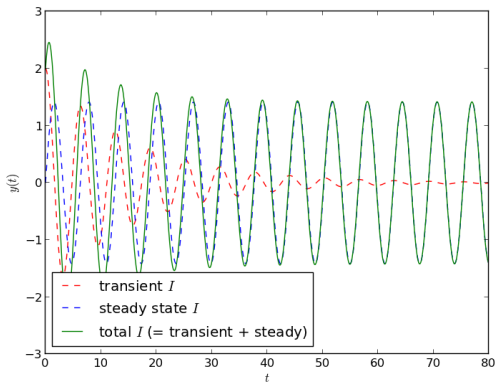

# Review!

Today:

- Forced vibrations

Next time:

- Review for second midterm

# Review!

Today:

- Forced vibrations

Next time:

- Review for second midterm

# Review!

Today:

- Forced vibrations

Next time:

- Review for second midterm

# Review!

Today:

- Forced vibrations

Next time:

- Review for second midterm